



**B.Sc. ELECTRONICS**  
**Third Semester**  
**ANALOG ELECTRONICS**  
**(BSE - 302)**

**Duration: 3Hrs.**

**Full Marks: 70**

Part-A (Objective) =20  
Part-B (Descriptive) =50

**(PART-B: Descriptive)**

**Duration: 2 hrs. 40 mins.**

**Marks: 50**

**Answer any four from Question no. 2 to 8**  
**Question no. 1 is compulsory.**

1. What are the different types of oscillator? Explain the working principle of oscillatory circuit. (4+6=10)
2. a) Explain the operation of RC coupled amplifier in middle frequency range.  
b) Explain the concept of virtual ground with the help of diagram. (6+4=10)
3. a) What are the various configurations of open loop OP-AMP? Discuss.  
b) Write short notes on CMRR. (6+4=10)
4. a) Derive the expression of out voltage for Summing amplifier.  
b) State Barkhausen criterion of oscillation. (6+4=10)
5. a) Derive the expression of gain in voltage-shunt feedback circuit.  
b) Write the advantages of negative feedback. (6+4=10)
6. a) What do you mean by Class C operation of power amplifier? Derive the expression of overall efficiency of Class B amplifier.  
b) A Class A power amplifier has zero signal power dissipation of 10 watt. If the a.c. output power is 3 watt, find
  - 1) collector efficiency.
  - 2) power rating of transistor.(1+5+4=10)



7. a) Explain the operation of Multistage amplifier.  
b) What is a Differentiator? Explain briefly.

(6+4=10)

8. a) Discuss the effect of negative feedback on input impedance in voltage-series feedback.  
b) A tuned collector oscillator makes use of an LC tuned circuit with  $L=58.6\text{H}$  and  $C=300\text{pF}$ . Calculate the frequency of oscillation.

(6+4=10)

\*\*\*\*\*





**B.Sc. ELECTRONICS**  
**Third Semester**  
**ANALOG ELECTRONICS**  
**(BSE - 302)**

**Duration: 20 minutes**

**Marks – 20**

**(PART A - Objective Type)**

**I. Choose the correct answer:**

**1×20=20**

1. A CE amplifier provides a phase reversal of input signal which is
  - a) 360 degree out of phase
  - b) 180 degree out of phase
  - c) 0 degree out of phase
  - d) 270 degree out of phase
2. If a Multistage amplifier consists of two amplifiers in cascade having gain  $A_1$  and  $A_2$ , then overall gain will be
  - a)  $A_1 * A_2$
  - b)  $A_1 + A_2$
  - c)  $A_1 - A_2$
  - d)  $A_1 / A_2$
3. In RC coupled amplifier, coupling components used are
  - a) resistor
  - b) capacitor
  - c) inductor
  - d) both resistor and capacitor
4. The effect of coupling capacitor in RC coupled amplifier is negligible in
  - a) high frequency range
  - b) middle frequency range
  - c) low frequency range
  - d) all the above
5. Regarding the negative feedback in amplifier which statement is wrong?
  - a) It widens the separation between 3-db frequencies.
  - b) It increases the gain bandwidth product.
  - c) It improves the gain stability.
  - d) It reduces distortion.
6. For a negative feedback, which statement is correct
  - a)  $A_F > A$
  - b)  $A_F < A$
  - c)  $A_F = A$
  - d) none of the above
7. An amplifier works as an oscillator in positive feedback, if
  - a)  $AB = 0$
  - b)  $AB = 1$
  - c)  $AB > 1$
  - d)  $AB < 1$
8. In RC-Coupled transistor amplifier, emitter bypass capacitor offers
  - a) low reactance path to signal
  - b) high reactance path to signal
  - c) does not affect input signal
  - d) all the above
9. In Voltage-shunt feedback, there is
  - a) voltage sampling plus current mixing
  - b) voltage sampling plus shunt mixing
  - c) current sampling plus shunt mixing
  - d) none of the above

10. In voltage series feedback, input resistance
- increases
  - decreases
  - remains same
  - none of the above
11. The reciprocal of sensitivity is called
- stabilization of gain
  - desensitivity
  - distortion
  - all the above
12. In Colpitt's Oscillator, the tank circuit consists of
- one inductor and two capacitors.
  - one capacitor and two inductors.
  - one inductor and one capacitor.
  - one inductor, one capacitor and one resistance.
13. The total phase shift in Hartley Oscillator is
- 360 degree
  - 180 degree
  - 180 degree
  - 0 degree
14. The gain of an Ideal OP-AMP is
- infinite
  - zero
  - one
  - all the above
15. In Inverting Amplifier, voltage gain is given by
- $-(R_F/R_I)$
  - $(R_F/R_I)$
  - $1+(R_F/R_I)$
  - $(R_F+R_I)$
16. Virtual ground implies that the potential difference between two terminal is
- zero
  - infinity
  - unity
  - none of the above
17. The CMRR value for an Ideal OP-AMP is
- zero
  - one
  - infinite
  - less than 1
18. Barkhausen criterion of oscillation is
- $AB=0$
  - $AB=1$
  - $AB=\infty$
  - none of these
19. Audio frequency range is given by
- 20 Hz to 200 Hz
  - 20 Hz to 20 KHz
  - 2 Hz to 20 KHz
  - 20 Hz to 20 MHz
20. In RC Coupled amplifier, the phase angle in each RC segment is
- 90 degree
  - 360 degree
  - 60 degree
  - 0 degree

\*\*\*\*\*